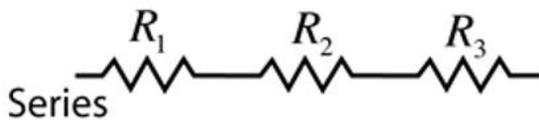


# Essential Circuit Rules

## RULE#1

When resistors are in series you can just add them together to get determine a total (or equivalent resistance)




$$R_{equivalent} = R_1 + R_2 + R_3 + \dots$$

$R_T = R_1 + R_2 + R_3 + \dots + R_n$   
 $R_T = 2\Omega + 5\Omega + 7\Omega$   
 $R_T = 14\Omega$
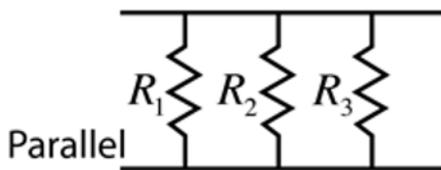
## RULE#2

When resistors are placed in parallel, this will you are essentially adding paths for electrons to flow. This will decrease the total resistance. You can find the total (or equivalent resistance) using the following formulas:




$$\frac{1}{R_{equivalent}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots$$

$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{4\Omega} + \frac{1}{4\Omega}$   
 $\frac{1}{R_T} = \frac{2}{4\Omega} \Rightarrow R_T = \frac{4\Omega}{2}$   
 $R_T = 2\Omega$

$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$   
 $\frac{1}{R_T} = \frac{1}{10} + \frac{1}{2} + \frac{1}{1}$   
 $\frac{1}{R_T} = \frac{1}{10} + \frac{5}{10} + \frac{10}{10}$   
 $\frac{1}{R_T} = \frac{1+5+10}{10} = \frac{16}{10} = 1.6$   
 $R_T (1/R_T) = 1.6 \times R_T$   
 $1 = 1.6R_T$   
 $R_T = 1 / 1.6 = 0.625\Omega$


For only two resistors connected in parallel, the equivalent resistance may be found by the product of the two values divided by the sum

$$R_T = \frac{R_1 R_2}{R_1 + R_2}$$

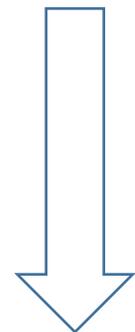

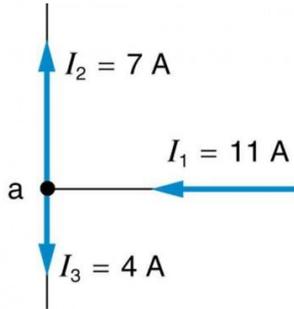
### RULE#3

**Current in = Current out.** Remember current is a flow of particles. When current comes to a juncture it splits. The total current entering the juncture must equal the total current exiting. **Conservation of mass!** This also means -no junction (or split) means no change in current.




$$I_1 = I_2 + I_3$$

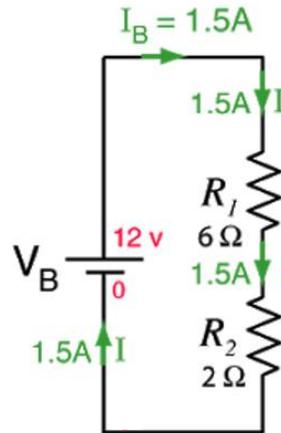

**No split** in this series circuit means the **current** always remains at **1.5A everywhere** in the circuit.

### RULE#4


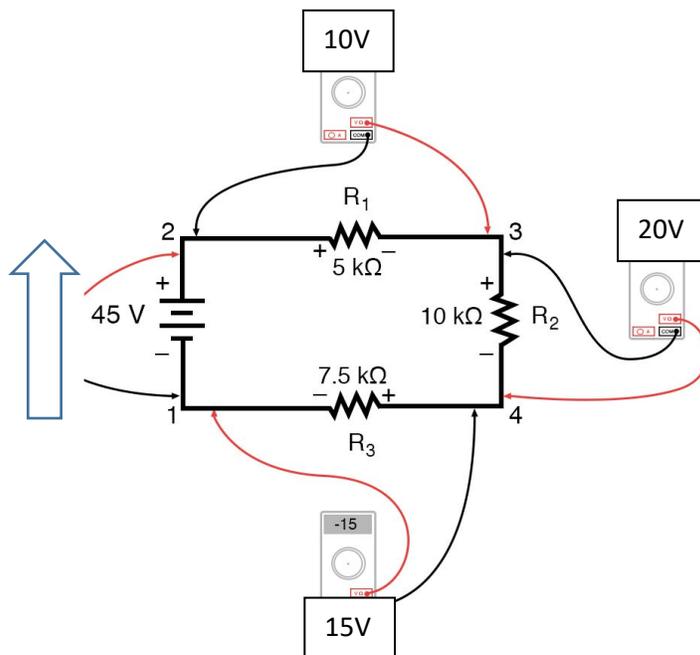
**Voltage in SERIES.** Remember Voltage is energy. If resistor are in series, the total voltage given to the circuit by the battery (or power source) **must be equal to all the losses in the series loop.** **Energy in = Energy out!**



$$45\text{Volts (supplied)} = V_1 + V_2 + V_3 \text{ (all voltage lost)}$$
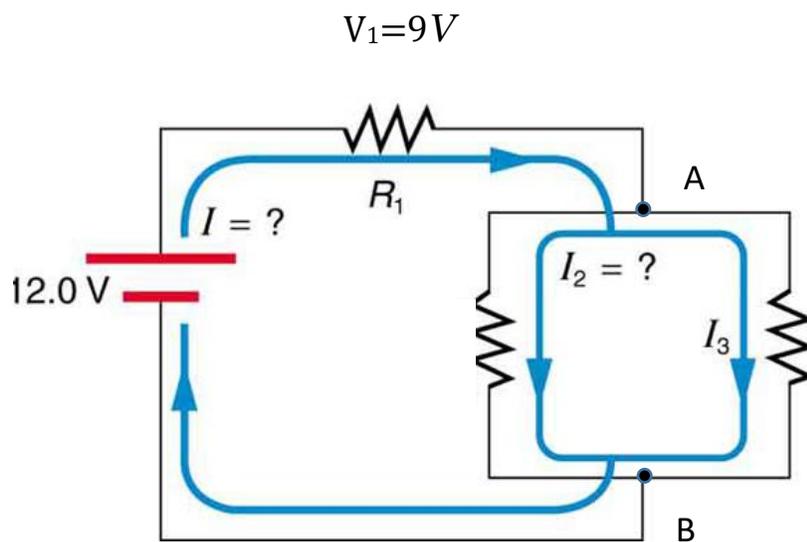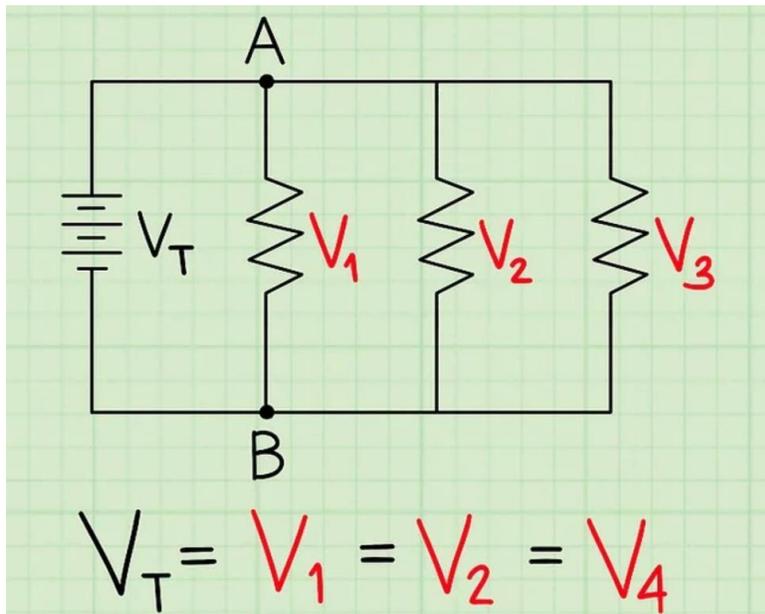
## RULE#5

**Voltage in Parallel.** Remember Voltage is **Joules PER Coulomb**. When resistors are in parallel (as shown below) the **voltage drop across any path will be the same**. Different amounts of current may flow in the different paths but (from start to finish) they all lose the same the same amount of **Joules PER COULOMB**.



$$V_2 = V_3 = 3V \text{ (from A to B)}$$

*Voltage drop is 3 volts  
Regardless of path taken  
From A to B*

*3 joules per coulomb must  
be lost.*